

|                                                                                   |                                                                                                                                                                                                   |                |                   |
|-----------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------------|-------------------|
| QP Code: D141275                                                                  |                                                                                                                                                                                                   | Total Pages: 1 | Name: 761772      |
|                                                                                   |                                                                                                                                                                                                   |                | Register No.      |
| SECOND SEMESTER (CUFYUGP) DEGREE EXAMINATION, APRIL 2026                          |                                                                                                                                                                                                   |                |                   |
| APPLIED PHYSICS / PHYSICS                                                         |                                                                                                                                                                                                   |                |                   |
| APH2CJ101 / PHY2CJ101: Electronics I                                              |                                                                                                                                                                                                   |                |                   |
| 2024 Admission onwards                                                            |                                                                                                                                                                                                   |                |                   |
| Maximum Time :2 Hours                                                             |                                                                                                                                                                                                   |                | Maximum Marks :70 |
| Section A                                                                         |                                                                                                                                                                                                   |                |                   |
| All Questions can be answered. Each Question carries 3 marks (Ceiling : 24 Marks) |                                                                                                                                                                                                   |                |                   |
| 1                                                                                 | What do you understand by extrinsic and intrinsic semiconductors?                                                                                                                                 |                |                   |
| 2                                                                                 | What are the limitations in the operating conditions of PN junction?                                                                                                                              |                |                   |
| 3                                                                                 | What are the different types of filter circuits used in rectifiers?                                                                                                                               |                |                   |
| 4                                                                                 | Define ripple factor? What is its value in the case of a full wave rectifier?                                                                                                                     |                |                   |
| 5                                                                                 | What do you mean by knee voltage?                                                                                                                                                                 |                |                   |
| 6                                                                                 | Which are the most commonly used semiconductors and why?                                                                                                                                          |                |                   |
| 7                                                                                 | What is a LED?                                                                                                                                                                                    |                |                   |
| 8                                                                                 | What are the specialties of a Zener diode?                                                                                                                                                        |                |                   |
| 9                                                                                 | Differentiate between Analog and Digital Signals ?                                                                                                                                                |                |                   |
| 10                                                                                | Explain BCD ?                                                                                                                                                                                     |                |                   |
| Section B                                                                         |                                                                                                                                                                                                   |                |                   |
| All Questions can be answered. Each Question carries 6 marks (Ceiling : 36 Marks) |                                                                                                                                                                                                   |                |                   |
| 11                                                                                | A half wave rectifier uses a transformer of a turn ratio 6:1. The load resistance is 800 $\Omega$ . If the primary voltage in rms is 240 V, find the DC output voltage and peak inverse voltage ? |                |                   |
| 12                                                                                | With a neat circuit diagram, Draw the input and output characteristics of a BJT in CE configuration                                                                                               |                |                   |
| 13                                                                                | Calculate the peak voltage across each half of a center-tapped transformer used in a full wave rectifier that has an average output voltage of 110 V ?                                            |                |                   |
| 14                                                                                | Define $\beta$ and derive a relation between $\alpha$ and $\beta$ ?                                                                                                                               |                |                   |
| 15                                                                                | Explain the meaning of faithful amplification with necessary diagrams?                                                                                                                            |                |                   |
| 16                                                                                | (i)Convert $(25)_{10}$ to Binary<br>(ii)Convert $(45)_{10}$ to Binary<br>(iii)Convert $(2A)_{16}$ to Decimal<br>(iv) Convert $(3F7)_{16}$ to Decimal                                              |                |                   |
| 17                                                                                | Draw the circuit diagram of a voltage doubler and explain the working ?                                                                                                                           |                |                   |
| 18                                                                                | In a common base connection, the current amplification factor is 0.9. if the emitte current is 1mA, find the value of the base current. ?                                                         |                |                   |
| Section C                                                                         |                                                                                                                                                                                                   |                |                   |
| Answer any ONE . Each Question carries 10 marks (1x10=10 Marks)                   |                                                                                                                                                                                                   |                |                   |
|                                                                                   |                                                                                                                                                                                                   |                |                   |
| 19                                                                                | Draw neat sketches of a half wave and a full wave rectifier and explain working?                                                                                                                  |                |                   |
| 20                                                                                | What do you mean by biasing of a transistor ? Describe any two methods for transistor biasing ?                                                                                                   |                |                   |